# Advanced Analysis Methods and Simulation tools for Noise in VCOs and PLLs

Jaijeet Roychowdhury

Amit Mehrotra

University of Minnesota

Berkeley Design Automation

#### Outline


- Basics of oscillator operation
- Perturbation analysis of oscillators: the PPV/NISF
- Phase noise and jitter basics
- Injection locking
- Oscillator/PLL jitter due to interference noise
- Phase noise examples and design guidelines
- PLL noise analysis and examples

## Basic Features of Oscillator Operation

## Why Oscillators are a Special Simulation Challenge

- Computation/size/accuracy: much greater than for amps/mixers
  - long startups, tiny timesteps needed
  - inefficient for even 1-transistor oscillators
  - integrated RF: 100s to 1000s of transistors
  - errors dependent on size of timesteps, integration method, ...
  - fundamental cause: marginal phase stability of all oscillators
    - numerical errors integrate over time
- Using SPICE directly for oscillator phase simulation should be avoided if you have alternatives

### Amplitude Stability and Nonlinearity

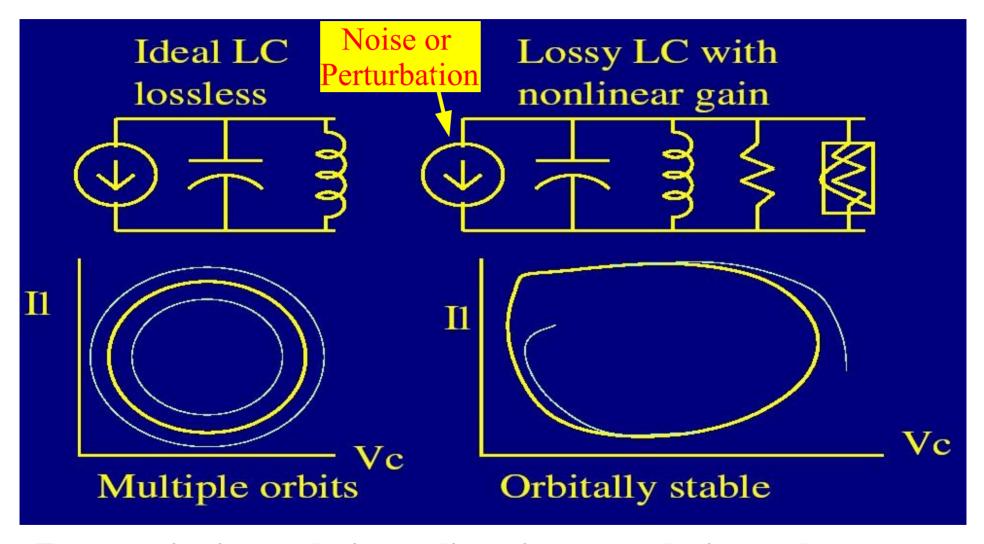

For **quantitative analysis**: <u>nonlinearity cannot be ignored</u> – fundamental to oscillator operation

## Perturbation Analysis of Oscillators

### Quantitative Perturbation Analysis

- Mathematically, circuits are <u>nonlinear</u> <u>differential equations</u>
  - Eg, for an RLC tank (using KCL and KVL):

$$\frac{\mathbf{d}}{\mathbf{dt}} \begin{bmatrix} v(t) \\ i(t) \end{bmatrix} = - \begin{bmatrix} C \\ L \end{bmatrix}^{-1} \begin{bmatrix} \frac{1}{R} & 1 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} v(t) \\ i(t) \end{bmatrix}$$

$$\dot{\mathbf{x}} = \mathbf{f}(\mathbf{x})$$

## Quantifying Oscillator Response


How does the oscillator (VCO) respond to "inputs"?

$$\dot{x}(t) = f(x) + \underbrace{b(t)}_{\text{input perturbation}}$$


- No perturbation  $\Rightarrow$  perfect periodic solution  $x_s(t)$
- Small b(t) perturbation:

$$x(t) = x_s(t + \underbrace{\alpha(t)}_{\text{growing phase error}}) + \underbrace{y(t)}_{\text{small}}$$

### Phase Response to Delta Function

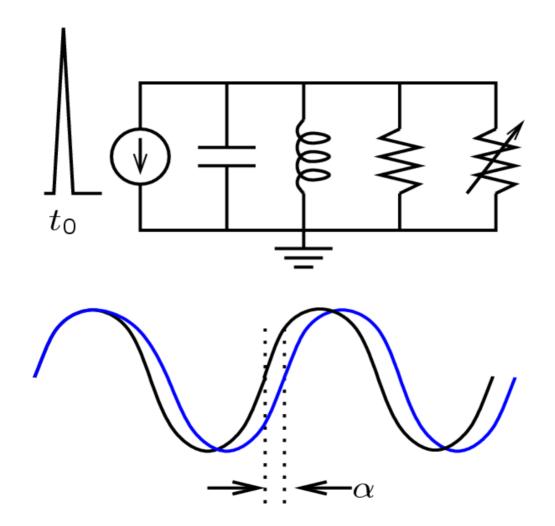

## Oscillator: Response to "Inputs"

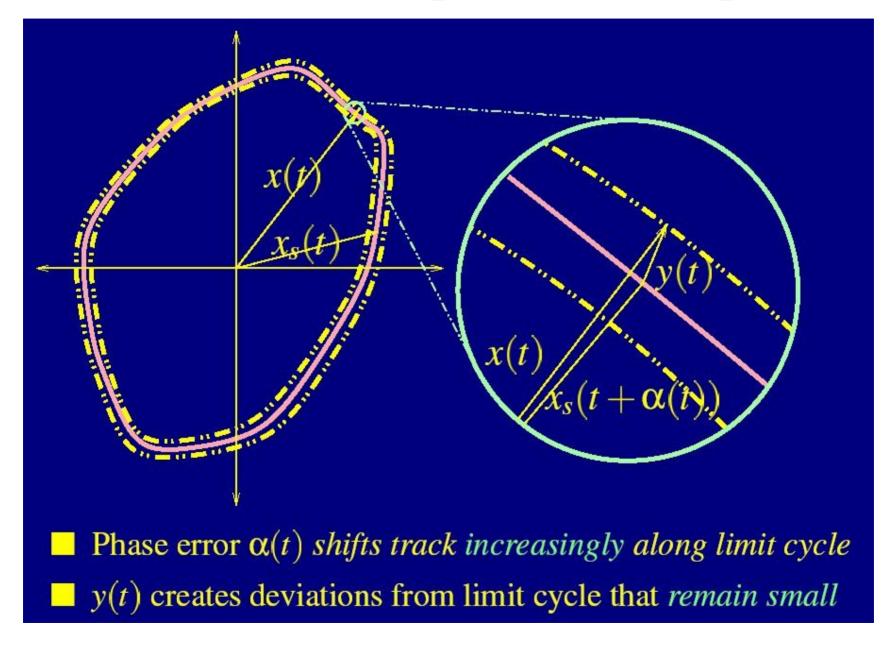

## Nonlinear Differential Equation for Phase

$$\dot{\alpha} = \mathbf{v}_1^{\mathbf{T}}(\mathbf{t} + \alpha(\mathbf{t})) \cdot \mathbf{b}(\mathbf{t})$$

- Simple differential equation governs phase
  - nonlinear (because PPV is periodic)
  - scalar (much smaller than oscillator equations)

[Demir Mehrotra Roychowdhury 97, 98, 01]

## The Perturbation Projection Vector (PPV): a *Nonlinear* ISF (NISF)

- v<sub>1</sub>(t): "nonlinear transfer or sensitivity function" relating "input" to oscillator phase response
  - (via nonlinear differential equation on previous slide)
  - v<sub>1</sub>(t): the PPV (Perturbation Projection Vector) or NISF (nonlinear ISF)
- In general, PPV/NISF does NOT equal the tangent vector of the phase plane plot
  - ie, not equal to the ISF [Hajimiri 98]
  - but <u>intuition is similar</u>: sensitivity of phase/jitter to external perturbations as a function of time

#### PPV/NISF vs the ISF

#### Similarities

- PPV/NISF and ISF identical for <u>high-Q negative</u> resistance oscillators
- (still important to use the NONLINEAR phase equation)

#### Differences


- PPV/NISF and ISF are <u>NOT IDENTICAL</u> for most other oscillators, including <u>ring oscillators</u>
- Applications where the difference matters (greatly):
  - Phase noise/jitter due to random noise
  - Injection locking
  - Jitter from interference noise (power/ground noise)

## Computing the PPV/NISF

- PPV/NISF can be computed efficiently from oscillator steady-state quantities
  - Find the periodic steady-state of oscillator
    - using, eg, HB, shooting, etc.
  - Various matrix computations
    - can be performed efficiently for large oscillators

[Demir Roychowdhury TCAD 03]
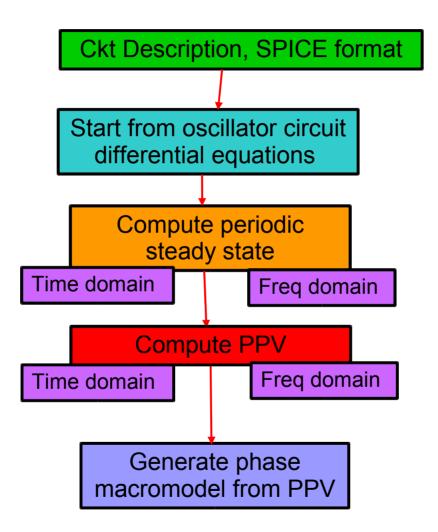
#### **PPV/NISF: Computation Techniques**



#### Phase Noise and Jitter


## Using the PPV/NISF to find jitter and phase noise spectrum

- Noise: perturbation to oscillator comes from thermal, shot, flicker noise sources
  - b(t) is **random** (eg, white Gaussian)
  - Now concerned with **noise power** (a.k.a noise variance)
- Phase deviation  $\alpha(t)$  now also random
  - Variance =  $E[\alpha^2(t)]$  is mean-squared jitter

#### Mean-squared Jitter

- Key result: <u>mean-squared jitter grows linearly</u> with time
  - $E[\alpha^2(t)] = ct$
  - (technically: random walk or Brownian motion)
  - c: growth rate of mean-squared jitter
    - Crucial scalar parameter
    - Depends on PPV/NISF <u>and</u> device (thermal/shot/etc) noises
    - Expression available for c [Demir et al TCAS-1 2000]
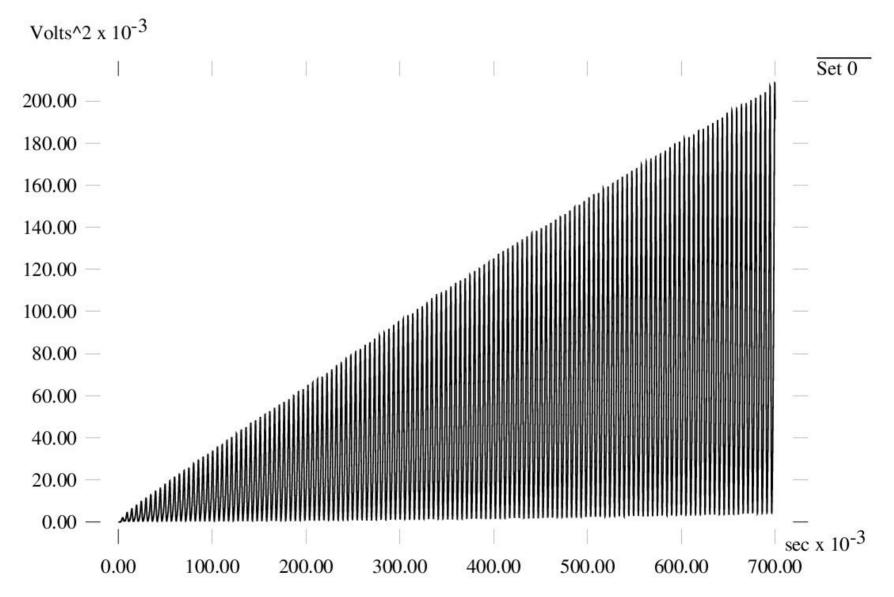
## Linear rise of mean-square jitter: Monte-Carlo simulation




#### Phase Noise Spectrum


- Measured spectrum is of voltage/current
  - of, eg,  $\sin(wt + \alpha(t))$ ; <u>not</u> of the phase  $\alpha(t)$  itself!
- Spectrum is directly related to jitter growth-rate
- Shape is **Lorenzian** broadens as **c** increases
  - No explosion at center frequency
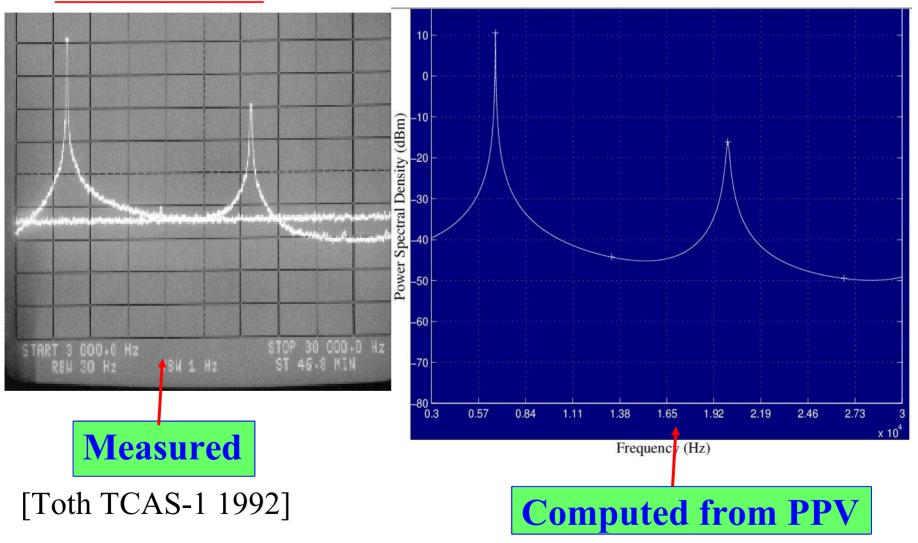
### Spectrum Does Not Explode at Carrier

PPV/NISF-based nonlinear theory resolves contradiction in Leeson's model


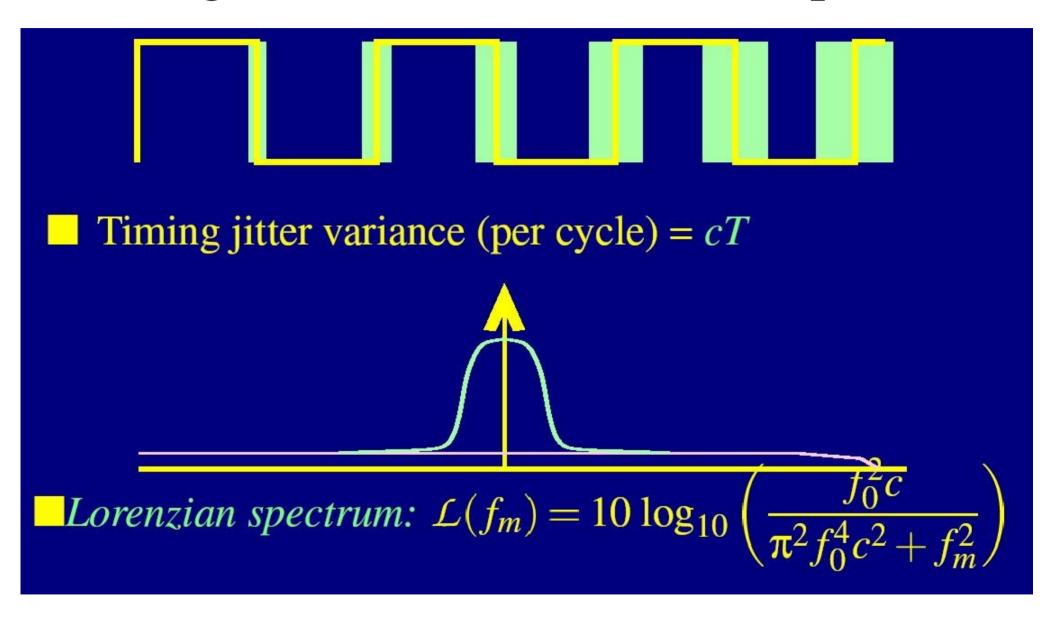
## Timing Jitter and Phase Noise Spectrum



## Injection Locking


#### **Injection Locking in Oscillators**

- Oscillator's frequency "locks" to frequency of external input
  - external frequency "over-rides" oscillator natural frequency
  - if frequencies close enough, even if input is very small
- Universal phenomenon: grandfather clocks, fireflies flashing, lasers, etc
- Impact: can be both good and bad
  - exploited in RF/mixed-signal design
  - undesired locking due to parasitic coupling a concern
- Can take extremely long to simulate in SPICE

### Predicting Injection Locking

- Find nonlinear phase error  $\alpha(t)$  due to b(t)
  - b(t) is now the <u>deterministic injection signal</u>
  - Use the nonlinear differential equation based on PPV/NISF to calculate  $\alpha(t)$ 
    - Linear equations don't work: injection locking is a fundamentally nonlinear phenomenon
  - If  $\alpha(t) = (w_1 w_0)t$ , the oscillator is injection locked
- Much faster/more accurate than SPICE simulation
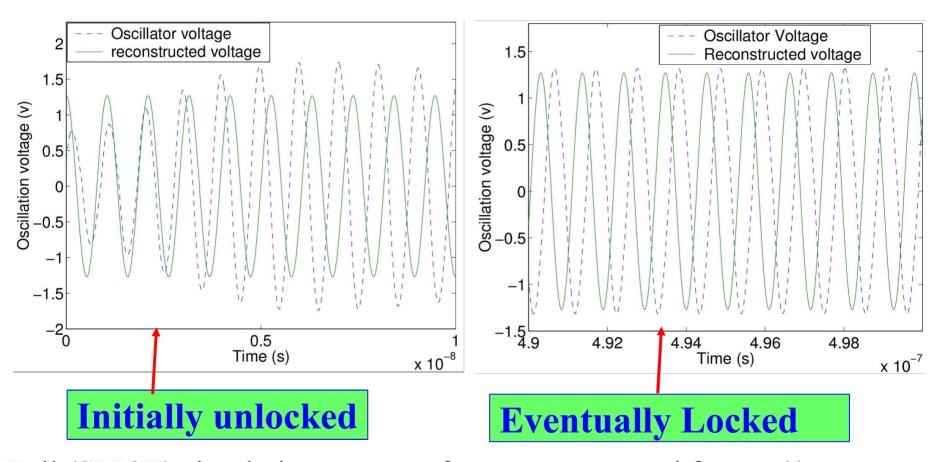
## Colpitts Oscillator: Injection Locking




Full (SPICE) simulation, vs waveform reconstructed from  $\alpha(t)$  (2 orders of magnitude speedup)

## Jitter Induced by Power/Ground Noise


#### Interference: "Deterministic Noise"

- Power/ground noise: not "truly" random
  - caused by interference from other circuits
  - not Gaussian, not stationary: "spikes" of noise
  - can be relatively large (15-20% of VDD)
- Use nonlinear phase equation (again)
  - deterministic input
  - PPV component supplies design insight

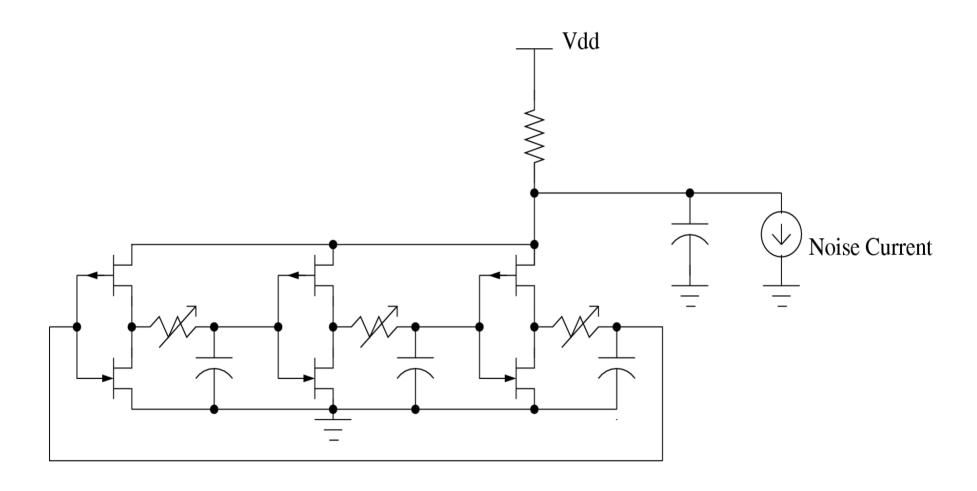
#### **Example: Simple Ring-Oscillator VCO**



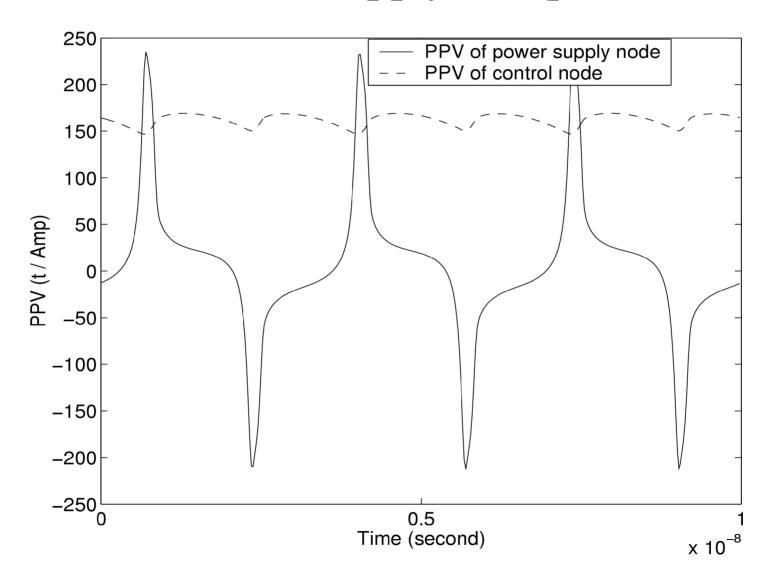
## VCO Perturbation Projection Vectors: Control Node and Power Supply Components



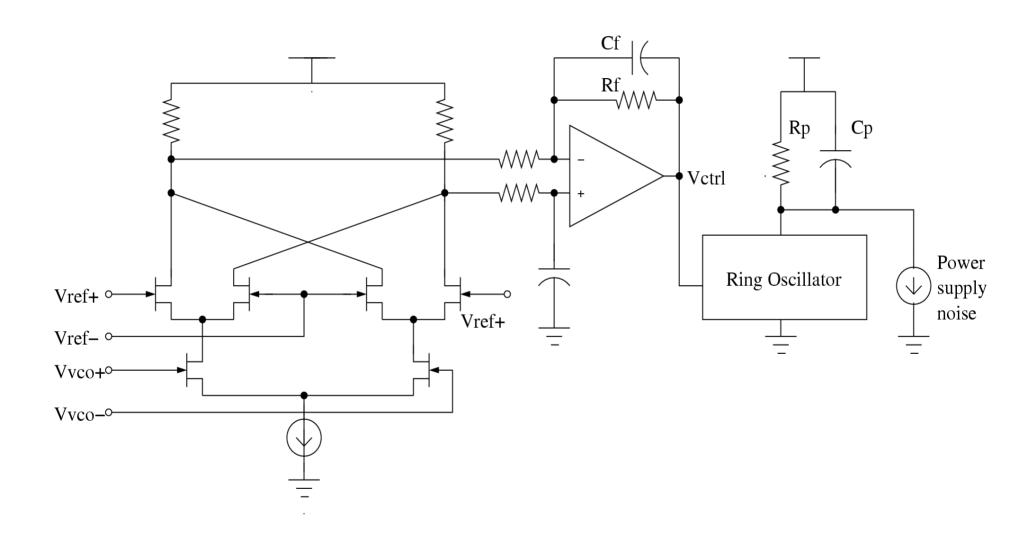
#### Simple Ring-Oscillator-based Phase-Locked Loop



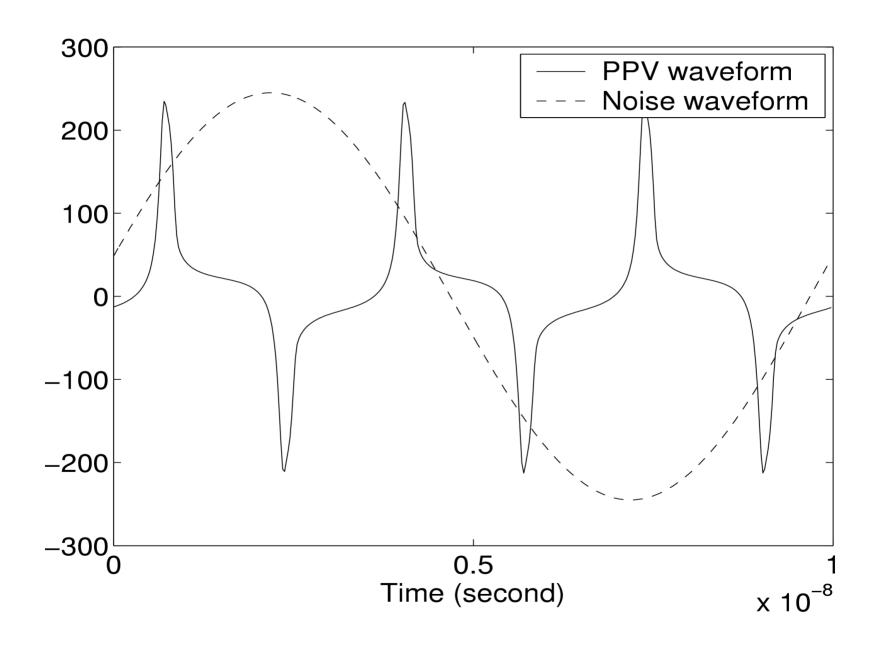
#### **Expected Impact of 1st harmonic Supply Noise**



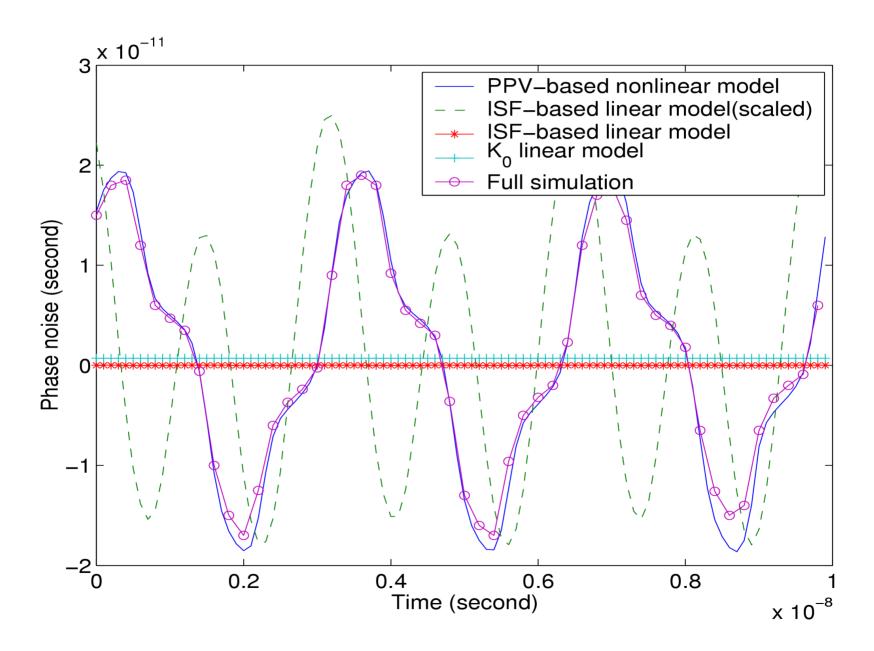
#### PLL Phase Reponse to Periodic Supply Noise


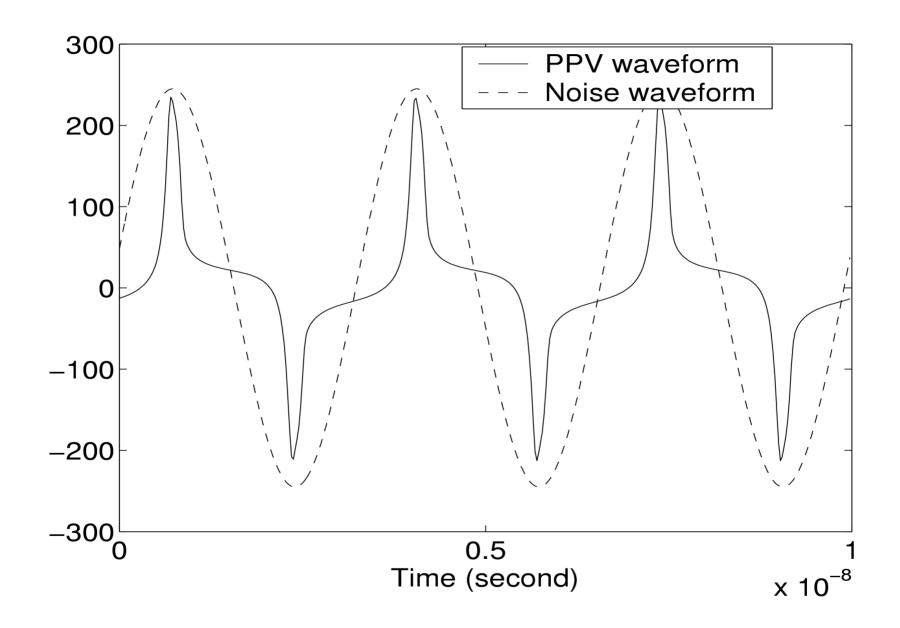
#### **Expected Impact of 3<sup>rd</sup> Harmonic Supply Noise**


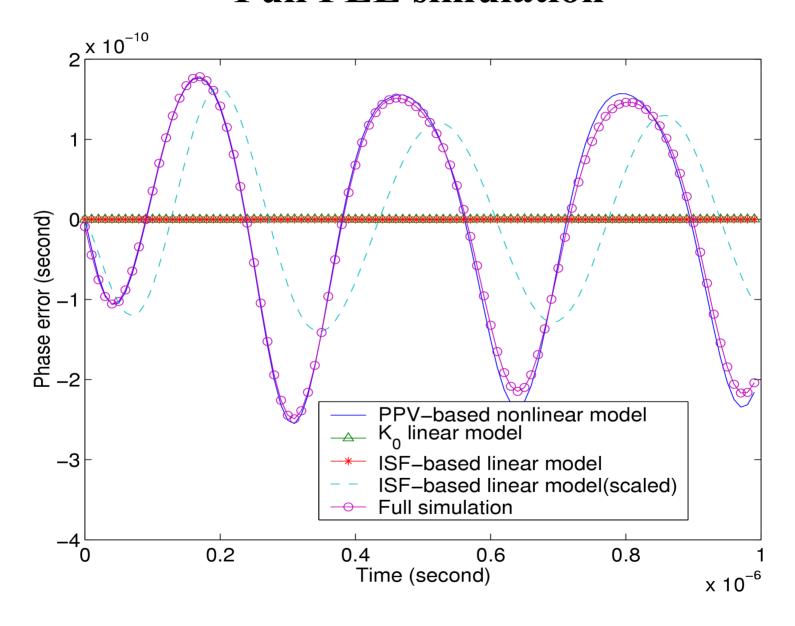
#### 3<sup>rd</sup> Harmonic Supply Noise: Phase Macromodel vs Full PLL simulation



#### References

- → K. Kundert, "Predicting the Phase Noise and Jitter of PLL-based frequency synthesizers", in the Designer's Guide (www.designersguide.com), Nov 2002.
- → J.L. Stensby, "Phase-locked Loops: Theory and Applications", CRC Press, New York, 1997.
- R. Adler, "A Study of Locking Phenomena in Oscillators", Proc. IRE, Vol 34, pp 351-357, June 1946.
- → A. Demir, A. Mehrotra and J. Roychowdhury, "Phase noise in oscillators: a unifying theory and numerical methods for characterization", IEEE Trans. Ckts Syst I Fundamental Theory and Applications, vol 47, no 5, pp 655-674, May 2000.
- → P. Vanassche, G. Gielen, W. Sansen, "Behavioural modelling of coupled harmonic oscillators", IEEE Trans. Computer-aided Design, vol 22, pp 1017-1026, Aug 2003.
- → M. Gardner, "Phase-Lock Techniques", Wiley, New York, 1966, 1979.
- → A. Hajimiri and T. Lee, "A general theory of phase noise in electrical oscillators", IEEE J. Solid State Ckts, vol 33, no 2, Feb 1998.
- → A. Demir, A. Mehrotra, and J. Roychowdhury, "Phase noise and timing jitter in oscillators", Proc CICC, May 1998.
- → J. Roychowdhury, "Automated Macromodel Generation for Electronic Systems", IEEE Behavioral Modeling and Simulation Workshop, Oct 2003.
- → A. Demir and J. Roychowdhury, "A Reliable and Efficient Procedure for Oscillator PPV Computation, with Phase Noise Macromodelling Applications", IEEE Transactions on Computer-Aided Design, Feb 2003.

#### References

- → X. Lai and J. Roychowdhury, "Capturing Oscillator Injection Locking via Nonlinear Phase-Domain Macromodels", IEEE J. Microwave Theory and Techniques, September 2004.
- → X. Lai and J. Roychowdhury, "Fast, Accurate Prediction of PLL Jitter Induced by Power Grid Noise", IEEE Custom Integrated Circuits Conference, Oct 2004.
- → P. Ghanta, Z. Li and J. Roychowdhury, "Analytical Expressions for Phase Noise Eigenfunctions of LC Oscillators", Proc. IEEE Asia South-Paci c Design Automation Conference, Jan 2004.
- → Payam Heydari, "Analysis of the PLL Jitter Due to Power/Ground and Substrate Noise," to appear in IEEE Trans. on Circuits and Systems I, 2005.